

CPE166 Lab 2 Part 1

By: Prof. Pang


Lab 2**Part 1: 3 By 3 Binary Combinational Array Multiplier**

The binary combinational multiplier diagram:

			X_2	X_1	X_0	
			Y_2	Y_1	Y_0	
			<hr/>			
			$X_2 Y_0$	$X_1 Y_0$	$X_0 Y_0$	
		$X_2 Y_1$	$X_1 Y_1$	$X_0 Y_1$		
	$X_2 Y_2$	$X_1 Y_2$	$X_0 Y_2$			
	<hr/>					
	P_5	P_4	P_3	P_2	P_1	P_0

Figure 1. 3 by 3 binary combinational multiplication diagram

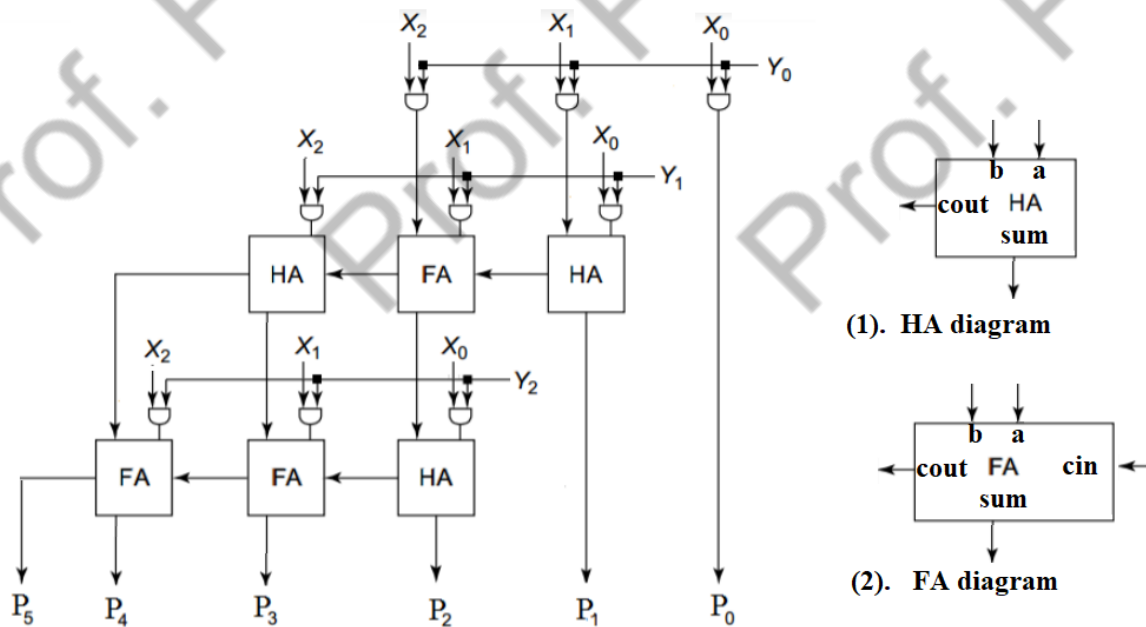This lab is to design the above multiplier by using the hardware structure shown below:



(3). Multiplier diagram

Figure 2. 3 by 3 binary combinational array multiplier hardware structure

CPE166 Lab 2 Part 1

By: Prof. Pang

Lab Procedure**Step 1. Half Adder Design**

The half adder adds two 1-bit binary inputs a and b. It generates two outputs, sum signal and carry cout signal.

Inputs		Outputs	
a	b	cout	sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0
Logic equations: $\text{cout} = a \cdot b$ $\text{sum} = a \oplus b$			

 


Figure 3. Half adder truth table, schematic and logic symbol

Design the above half adder circuit using Verilog, write testbench and run simulations. Verify that your simulation results are the same as the values listed in the truth table above.

CPE166 Lab 2 Part 1

By: Prof. Pang

Step 2. Full Adder Design

The full adder circuit adds three 1-bit binary inputs a, b and cin. It generates two outputs, sum signal and carry cout signal.

Inputs			Outputs	
a	b	cin	cout	sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Logic equations:
 $\text{sum} = a \oplus b \oplus \text{cin}$
 $\text{cout} = (a \oplus b) \text{cin} + a b$

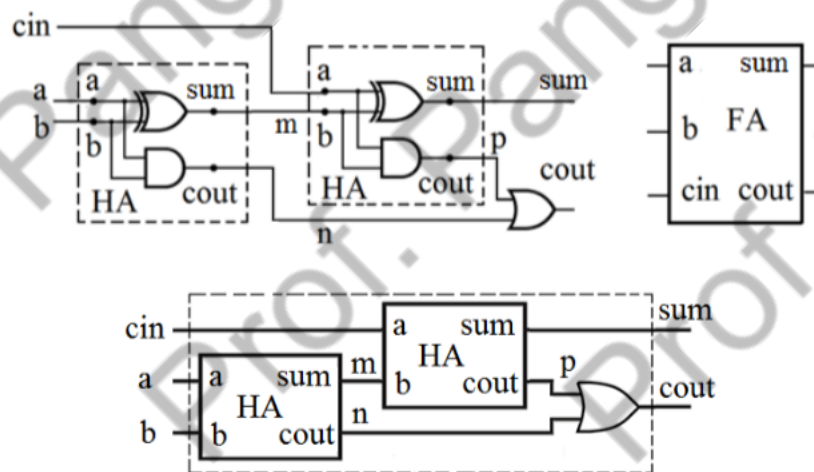


Figure 4. Full adder truth table, schematic and logic symbol

Design the above full adder circuit by using two half adder HA modules, and one OR gate in Verilog, write testbench and run simulations. Verify that your simulation results are the same as the values listed in the truth table above.

CPE166 Lab 2 Part 1

By: Prof. Pang

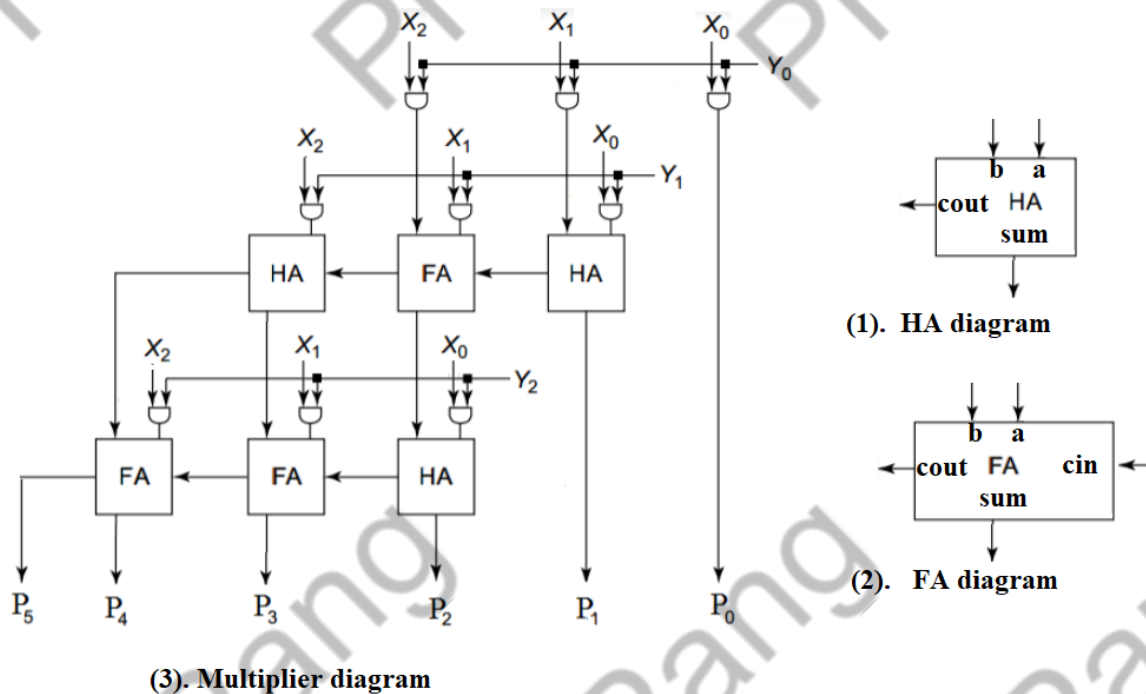
Step 3. Final Combinational Multiplier Design

Figure 5. 3 by 3 combinational array multiplier schematic

Design the above multiplier circuit by using nine AND gates, three half adder HA modules and three full adder FA modules in Verilog, write a testbench and run simulation.

Demo Requirement

You need to demonstrate the final simulation waveform of the multiplier design to your lab instructor.

You need to download this design to the FPGA board and demonstrate it to your lab instructor.

CPE166 Lab 2 Part 1

By: Prof. Pang

Note: Before starting this experiment, all the necessary knowledge required to complete this work has been introduced in the CPE166 lecture session. The following examples are for you to refresh your learning.

Sample Verilog Codes:

```
module ex1( a, b, f1, f2, f3, f4);
```

```
input a, b;
```

```
output f1, f2, f3, f4;
```

```
assign f1 = a ^ b;           // xor gate
```

```
assign f2 = a ^~ b;         // xnor gate
```

```
assign f3 = ~( a & b );     // nand gate
```

```
assign f4 = ~( a | b);      // nor gate
```

```
endmodule
```

```
module ex2( a, b, c, f );
```

```
input a, b, c;
```

```
wire m, n;
```

```
output f;
```

```
assign m = ~a ;             // not gate
```

```
assign n= b & c ;           // and gate
```

```
assign f = m | n;           // or gate
```

```
endmodule
```

```
`timescale 1ns/1ps
```

```
module ex2_tb;              //testbench for ex2 design
```

```
reg a, b, c;
```

```
wire f;                     // Only a, b, c and f are used for testing.
```

```
integer k;
```

```
ex2 g1(a, b, c, f);
```

CPE166 Lab 2 Part 1

By: Prof. Pang

initial

begin

```
$monitor($time, " ns, a=%b, b=%b, c=%b, f=%b", a, b, c, f);
```

```
for (k=0; k<8; k=k+1)
```

```
begin
```

```
{a, b, c} = k;
```


```
#5;
```

```
end
```

```
#5 $stop;
```

```
end
```

```
endmodule
```

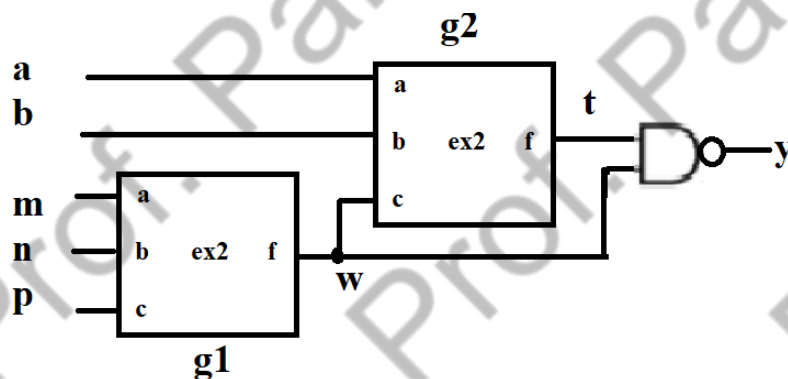Sample Circuit:**Sample Implementation in Verilog:**

```
module sample (a, b, m, n, p, y);
```

```
input  a, b, m, n, p;
```

```
output y;
```

```
wire  w, t;
```

```
ex2  g1 ( .a (m), .b(n), .c(p), .f(w) );
```

```
ex2  g2 (.a (a), .b(b), .c(w), .f (t) );
```

```
assign y = ~( w & t);
```

```
endmodule
```