 


Lab 3

Part 1: Seven Segment Display

Utilize four input switches and one seven-segment display device on the FPGA board to show numbers 0 through 9.

For example, if the binary value of the four input switches is “0011”, then the decimal number 3 should be displayed on the seven-segment display device.



Demo:

You need to download your SystemVerilog design on the FPGA board and show the result to your lab instructor.

CPE166 Advanced Logic Design

Lab 3 Part 1

By Prof. Pang

SystemVerilog

In SystemVerilog, you can use “logic” to replace both “wire” and “reg”. You can utilize “always_comb” for designing combinational logic circuit. SystemVerilog is a superset of Verilog and is compatible with it.

Sample SystemVerilog Syntax

```
module mycir ( input logic [1:0] a, output logic [3:0] f );
always_comb
case(a)
2'b00: f = 4'b0001;
2'b01: f = 4'b0010;
2'b10: f = 4'b0100;
2'b11: f = 4'b1000;
default: f = 4'b0000;
endcase

endmodule
```

```
module svinv_tb;
logic [1:0] a;
logic [3:0] f;

mycir uut(a, f);

initial begin
for(int i= 0; i<= 3; i++)
begin
a = i;
#5;
end
#10 $stop;
end

endmodule
```