

Lab 3**Part 4: Stopwatch Design**

This project is to design a stopwatch in VHDL by using the hierarchical design approach shown in the figure below.

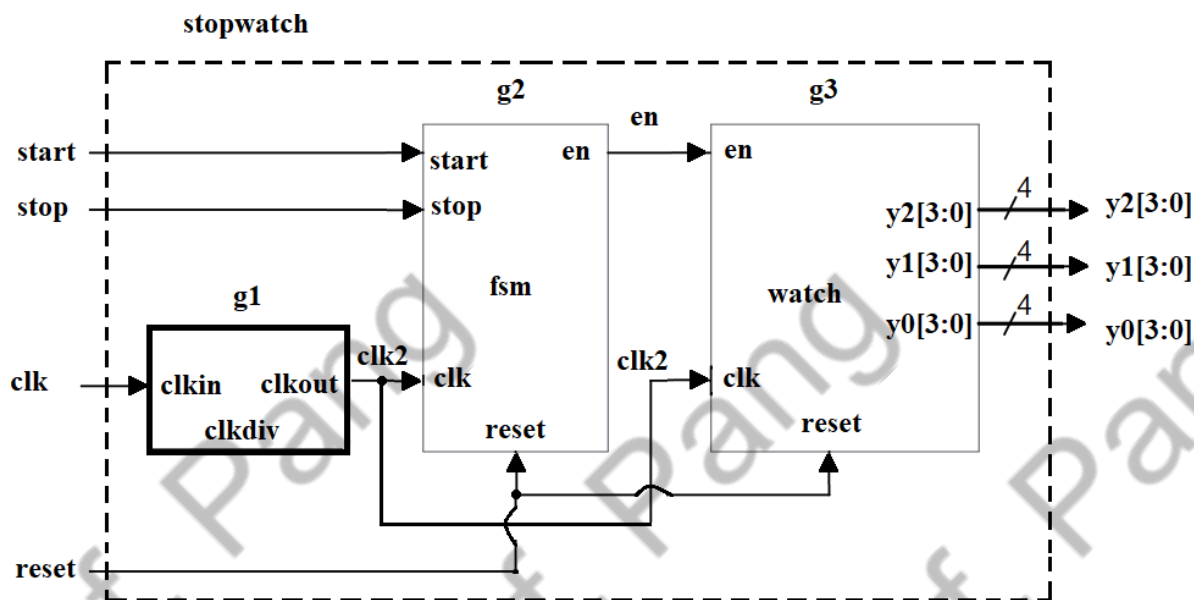


Figure 1. Stopwatch block diagram

The top-level I/O ports used in this design are shown below.

Table 1. I/O ports for the stopwatch design

Port Names	Port Direction	Port Size
start	Input	1
stop	Input	1
clk	Input	1
reset	Input	1
y3	Output	4
y2	Output	4
y1	Output	4
y0	Output	4

CPE166 Lab 3 Part 4

By: Prof. Pang

The stopwatch design has the following features:

- 1). The frequency of the input "clk" signal is 4 Hz.
- 2). At any time, if the "reset" input is logic high, the output of the stopwatch will be zero.
- 3). When the "start" input is logic high, the stopwatch will start counting.
- 4). When the "stop" input is logic high, the stopwatch will stop, but the stopwatch output will maintain its value. After that, when the "start" input is logic high again, the stopwatch will resume counting from its old value.
- 5). The output $y_2 y_1 y_0$ is a 3-digit binary number, and each digit ranges from 0 to 9.

Assuming $y_2 = (0110)_2 = 6$, $y_1 = (0101)_2 = 5$, $y_0 = (0111)_2 = 7$, this means 657 seconds.

If you press the "stop" button, the stopwatch will stop at 657 seconds and keep the value unchanged. After pressing the "start" button, the stopwatch will continue counting every second until: $y_2 = (1001)_2 = 9$, $y_1 = (1001)_2 = 9$, $y_0 = (1001)_2 = 9$, which means 999 seconds. After 999 seconds, the stopwatch will return to 0 and then increase its value every second.

Demo Requirement

You need to demonstrate the final simulation waveform of the stopwatch.vhd design to your lab instructor.

CPE166 Lab 3 Part 4

By: Prof. Pang

Lab Procedure**Step 1. clkdiv Block**

The clkdiv block gets the 4 Hz input clk_{in} signal and generates the 1 Hz output clk_{out} signal.

Design clkdiv.vhd and write a testbench to check your simulation results. The simulation waveform only needs to confirm that the output frequency is 4 times smaller than the input frequency.

Step 2. fsm Block

When the reset signal is logic high, the state machine enters the first idle state. Idle state means that the current watch is not counting, and the displayed output value is 0. Output "en" as 0 to disable counting. This can be represented in the state diagram below.

 


Figure 2. IDLE state of the fsm block

Figure 2 shows the state diagram of the idle state. In the idle state, the watch enable signal "en" is logic 0. If the "stop" button is pressed, the next state will still be the idle state. If the "start" button is pressed, the finite state machine needs to enter another state.

You can add more states to this design. In each state, you need to determine which state will become the next state based on the input signal values of "start", and "stop". In addition, you need to determine the output value of "en" based on whether you enable the watch to count or not.

To complete this step, you need to write fsm.vhd and testbench for simulation.

Step 3. watch Block

The watch block has three inputs: reset, en and 1 Hz clk. It has three 4-bit outputs: y₂, y₁, and y₀.

- 1). When "reset" is logic high, the watch will output 0.
- 2). Only when "en" is logic high, the watch will increase its value every 1 second.
- 3). Each of the y₂, y₁ and y₀ signals ranges from (0000)₂ to (1001)₂.

CPE166 Lab 3 Part 4

By: Prof. Pang

For example, if $y_2 = (0001)_2$, $y_1 = (1001)_2$ and $y_0 = (1001)_2$ at the current time, it means 199 seconds. After another 1 second, the watch needs to output $y_2 = (0010)_2$, $y_1 = (0000)_2$ and $y_0 = (0000)_2$ which means 200 seconds.

To complete this step, you need to write watch.vhd and testbench for simulation.

Step 3. Final stopwatch Block

The final stopwatch design is shown in Figure 1, with four 1-bit inputs, including reset, clk, start and stop, and three 4-bit outputs, including y_2 , y_1 , and y_0 .

In the architecture part of the design, two internal signals must be declared, including "en" and "clk2", and three components must be declared, including clkdiv, fsm and watch.

In addition, the main design part requires a clkdiv instance, an fsm instance and a watch instance. The two internal signals "en" and "clk2" are used for wiring of different modules.

Complete the final design and write testbench for simulations.

CPE166 Lab 3 Part 4

By: Prof. Pang

Note: Before starting this experiment, all the necessary knowledge required to complete this work has been introduced in the CPE166 lecture session. The following examples are for you to refresh your learning.

Sample VHDL Codes:

-- clk division circuit: divide by 8

Library ieee;

Use ieee.std_logic_1164.all;

use ieee.std_logic_unsigned.all;

use ieee.std_logic_arith.all;

entity example1 is

port (clkin: in std_logic;

clkout: out std_logic

);

end example1;

architecture arch1 of example1 is

signal cnt: std_logic_vector (3 downto 0) := "0000";

begin

process(clkin)

begin

if (rising_edge(clkin)) then

if (cnt = 7) then

cnt <= (others=>'0');

clkout <= '1';

elsif (cnt < 3) then

cnt <= cnt + 1;

clkout <= '1';

else

cnt <= cnt + 1;

clkout <= '0';

CPE166 Lab 3 Part 4

By: Prof. Pang

```
        end if;
    end if;

    end process;

end arch1;


library IEEE;
use IEEE.std_logic_1164.all;

entity testbench is
end testbench;

architecture tb of testbench is
    component example1
        port ( clkin: in std_logic;
              clkout: out std_logic
            );
    end component;
    signal clkin, clkout: std_logic;
    begin
        DUT: example1 port map(clkin, clkout);

        clocking: process
        begin
            clkin <= '0';

            wait for 5 ns;

            clkin <= '1';

            wait for 5 ns;

        end process;

        End tb;
```

CPE166 Lab 3 Part 4

By: Prof. Pang

Sample VHDL Codes:

-- General counter: counting from 0 to 18 and then repeat.

Library ieee;

Use ieee.std_logic_1164.all;

use ieee.std_logic_unsigned.all;

use ieee.std_logic_arith.all;

entity example2 is

port (clk: in std_logic;

dout: out std_logic_vector(4 downto 0)

);

end example2;

architecture arch2 of example2 is

signal cnt: std_logic_vector (4 downto 0) := "00000";

begin

process(clk)

begin

if (rising_edge(clk)) then

if (cnt = 18) then

cnt <= (others=>'0');

else

cnt <= cnt + 1;

end if;

end if;

end process;

dout <= cnt;

end arch2;

CPE166 Lab 3 Part 4

By: Prof. Pang

library IEEE;

use IEEE.std_logic_1164.all;

entity testbench is

end testbench;

architecture tb of testbench is

component example2

port (clk: in std_logic;

dout: out std_logic_vector(4 downto 0)

);

end component;

signal clk: std_logic;

signal dout: std_logic_vector(4 downto 0);

begin

DUT: example2 port map(clk, dout);

clocking: process

begin

clk <= '0';

wait for 5 ns;

clk <= '1';

wait for 5 ns;

end process;

end tb;